

Experiment no: 08

Name of the experiment: Control a high voltage load using mechanical relay.

objective(s):

1. To learn how to interface ac load through relay with PIC microcontroller.
2. To design and operate the circuit of relay interfacing.

Theory: An electronic switch means is relay, using low power circuits. Relay isolates low power circuits from high power circuits. It is activated by energizing coil wound on a soft iron core. A relay should not be directly connected to a microcontroller.

Because -

1. A microcontroller is not able to supply current required for the working of relay. Maximum current that a PIC microcontroller handle is 25 mA while a relay needs about 50-100 mA current.

2. A relay is activated by energizing its coil. Microcontroller may stop working by the negative voltages produced in the relay due to its back emf.

Apparatus required: PIC16F877A, crystal, capacitors, resistor, transistor, diode, relay, ac voltage.

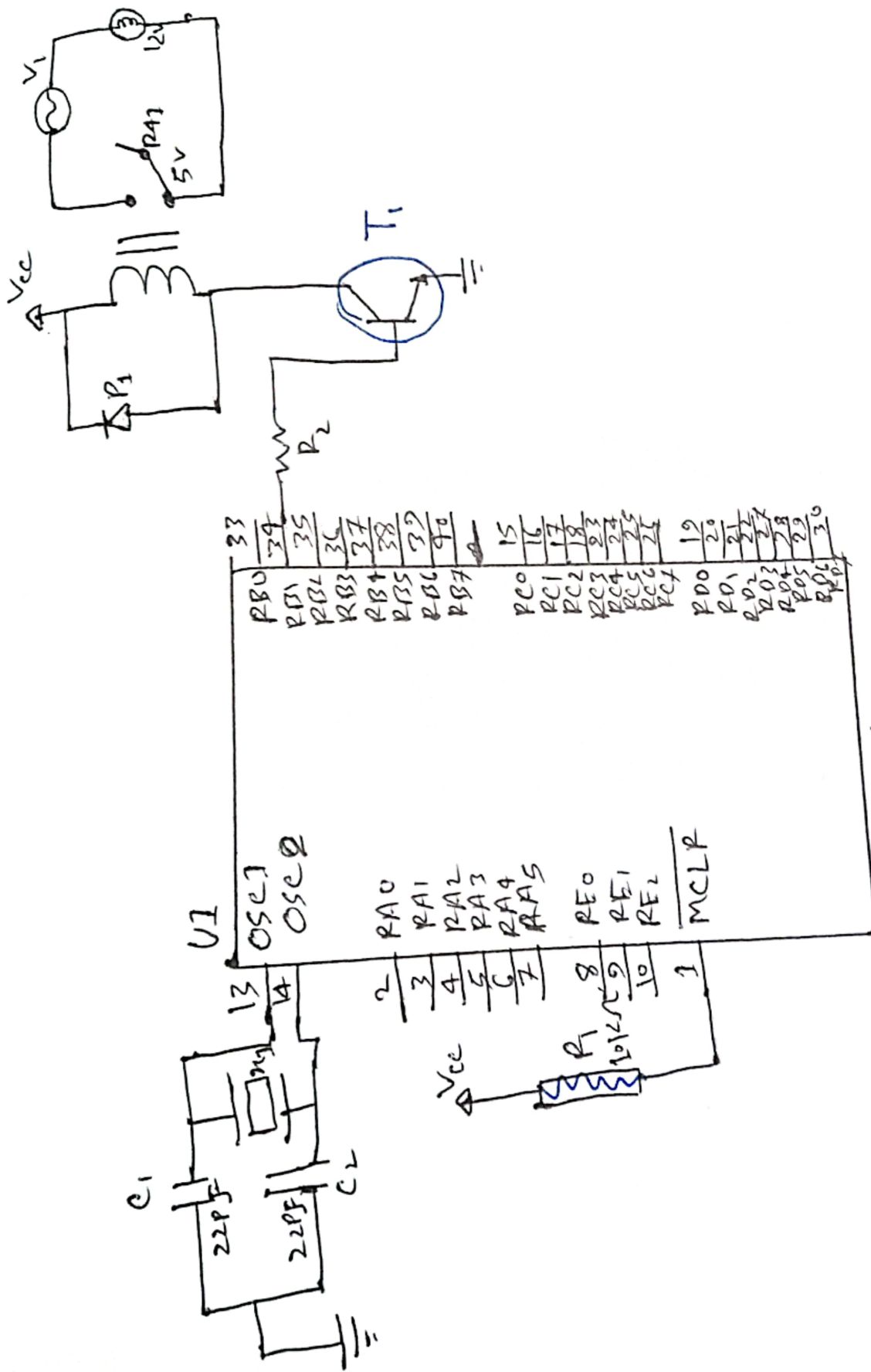


FIG 1 A high voltage load control using mechanical relay.

source code)

```
void main()
```

```
{
```

```
    TRISB = 0X00;
```

```
    PORTB = 0X00;
```

```
    while(1)
```

```
    {
```

```
        PORTB.F0 = 1;
```

```
        delay_ms(2000);
```

```
        PORTB.F0 = 0;
```

```
        delay_ms(2000);
```

```
    }
```

```
}
```

